

- This is an individual assignment. Please do not collaborate.
- If you think that this document does not clearly describes the assignment, ask questions before its too late.

For this assignment, you are expected to write a program which simulates a logic circuit for a set of given inputs.

In this assignment, you are going to use structure and dynamic memory allocation.

Be careful with file names. You won't given a chance to correct any mistakes.

- Your program reads two files:
 - `circuit.txt`
 - `input.txt`
- Your program creates a text file:
 - `output.txt`
- According to content in `circuit.txt`, the program **dynamically** creates necessary structures for a logic circuit and evaluates the cases listed in `input.txt`.
- Your program prints the output to `output.txt`. Each output step should be on a separate line.

circuit.txt

- Each line starts with a **keyword**. Possible keywords:
 - INPUT
 - AND
 - OR
 - NOT
 - FLIPFLOP
- The first line specifies input labels. Labels are separated by spaces. Example:


```
INPUT a input2 c3 k
```
- Here there are 4 inputs are defined. Each has an identifier. `a`, `input2`, `c3`, `k`.
- AND keyword specifies that there is an **and** gate defined. AND keyword follows the identifier for the gate and two other identifiers for the inputs. Example:


```
AND gate_A c3 another_id
```
- Here the **and** gate is identified by the string `gate_A`. Its inputs are identified `c3` and `another_id`. These identifiers can be input identifiers or identifiers for other gates.
- OR keyword specifies that there is an **or** gate defined. OR keyword follows the identifier for the gate and two other identifiers for the inputs. Example:


```
OR gate_B ck id3
```
- Here the **or** gate is identified by the string `gate_B`. Its inputs are identified `ck` and `id3`. These identifiers can be input identifiers or identifiers for other gates.

- NOT keyword specifies that there is an **not** gate defined. NOT keyword follows the identifier for the gate and one other identifier for its input. Example:

```
NOT gate_C c5
```

- Here the **not** gate is identified by the string **gate_C**. It has only one input and it is identified by the string **c5**.
- FLIPFLOP keyword specifies that there is an **flip-flop** gate defined. FLIPFLOP keyword follows the identifier for the gate and one other identifier for its input. Example:

```
FLIPFLOP gate_F c6
```

- Here the **flip-flop** gate is identified by the string **gate_F**. Its input is identified by **c6**.

input.txt

- Each line is a list of 1 and 0. Example:

```
1 0 1 1
0 1 1 1
0 0 1 0
1 0 0 1
```

Example:

- Suppose that **circuit.txt** has the following content:

```
INPUT a b c d
AND and1 a b
OR or1 and1 c
NOT n1 d
FLIPFLOP f1 n1
AND a2 or1 f1
```

- **input.txt** has the following content:

```
1 1 0 1
1 0 1 0
1 1 1 0
```

- Assume that initially **former-out** of any FLIPFLOP is 0.
- Any FLIPFLOPs should preserve the state throughout the evaluation of the whole **input.txt**.
- Each line in **input.txt** is assigned to identifiers **a**, **b**, **c**, **d**, defined in **circuit.txt**. According to the truth tables, outputs of gates are calculated.
- For the **input.txt** given, the contents of **output.txt** should be:

```
0
1
0
```

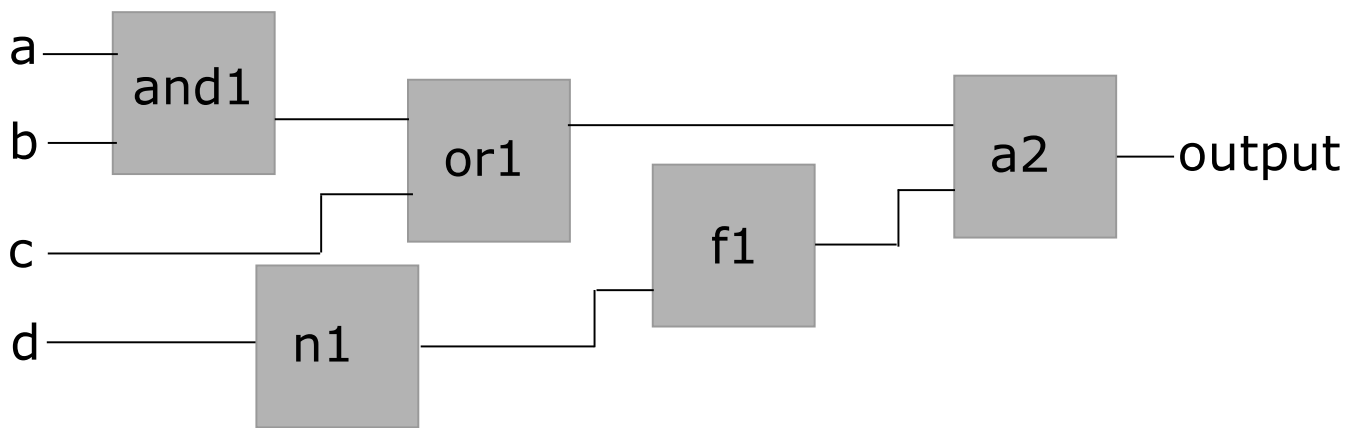


Figure 1: Example Logic Circuit

Remarks

- Output is not defined explicitly. It is your job to figure out the output pin. There will always going to be one output pin.
- Each identifier is unique. Max length of each identifier is 10 chars.
- Assume there won't be multiple spaces separating the identifiers, keywords or data. Tokenize it according to this assumption.
- There won't be any errors in the files.
- You **have to** use **dynamical memory allocation** and **struct**. You **have to** use **struct** in order to represent the gates of the circuit.
- Do not submit your code without testing it with several different scenarios. Try cases with multiple gates of the same type. Try cases with single gate. Try `input.txt` with thousands of lines. Try cases with many gates. Try cases where there are many inputs.
- You can use **c structs**, unions, arrays, c strings, pointers, recursion.
- Write comments in your code.
- Do not print anything to `stdout` and `stderr`.
- Do not submit any of the files you used for testing.
- Do not submit your output file.

Truth Tables:

- AND

a	b	out
0	0	0
0	1	0
1	0	0
1	1	1

- OR

a	b	out
0	0	0
0	1	1
1	0	1
1	1	1

- NOT

a	out
0	1
1	0

- FLIPFLOP

a	former_out	out
0	0	0
0	1	1
1	0	1
1	1	0